



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : L 60640

B.E./B.Tech. DEGREE EXAMINATIONS, NOV./DEC. 2020

Second Semester

Civil Engineering

GE 2151/EE 1153/10133 EE 206/080280011/EE 26 – BASIC ELECTRICAL AND

ELECTRONICS ENGINEERING

(Common to all Branches)

(Regulations 2008/2010)

(Also Common to 10133EE206 for B.E.(Part-Time) First Semester-Mechanical Engineering-Regulations 2010)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A

(10×2=20 Marks)

1. Define R.M.S. value of an alternating quantity.
2. Name the essential torques required for the proper operation of indicating instrument.
3. A dc shunt generator supplies a load of 10 kW at 220 V through feeders of resistance 0.1Ω . The resistance of armature and shunt field windings is 0.05Ω and 100Ω respectively. Calculate the terminal voltage.
4. In a single phase transformer, $N_p = 350$ turns, $N_s = 1050$ turns, $E_p = 400$ V. Find E_s .
5. Give the applications of Zener Diode.
6. What are the different modes of transistor operation ?
7. Define Flip flop. What are the different types of flip-flop.
8. Mention the types of Analog to Digital converter.
9. As related to amplitude modulation, what is over modulation, under modulation and 100% modulation ?
10. Why are digital signals said to be noise immune ?



PART – B

(5×16=80 Marks)

11. a) Using Mesh Analysis, find the current through various branches in the circuit of figure 11 a. (16)

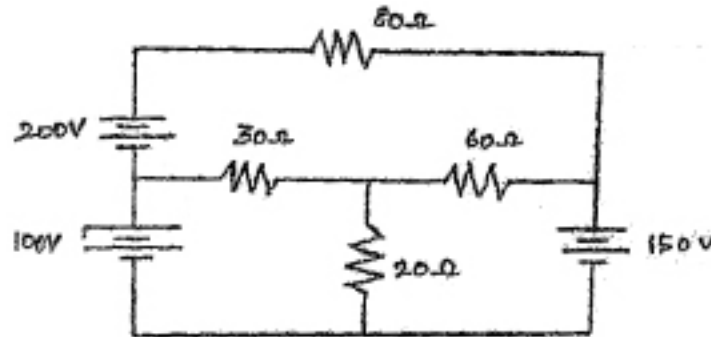


Figure : 11 (a)

(OR)

- b) Derive the expression for phase angle in the R-L series circuit R-C series circuit and R-L-C series circuit. (16)
12. a) A 220-V D.C. series motor runs at 700 rpm when operating at its full-load current of 20 A. The motor resistance is 0.5Ω and the magnetic circuit may be assumed unsaturated what will be the speed if :
- Load torque is increased by 44% ?
 - Motor current is 10 A.
 - Explain the operation and Principle of a DC motor.

(OR)

- b) Explain the construction of single phase transformer.
13. a) Describe the working of a PN junction diode with neat diagrams. Also explain its V-I Characteristics. (16)

(OR)

- b) Explain the working of the CB configuration of a BJT. (16)

14. a) i) 1) Reduce the following expressions using Boolean algebra postulates :
- $$\rightarrow a'b'c' + a'b'c + ab'c' + abc$$
- $$\rightarrow [(A + B)' + C]'$$
- (4)
- 2) Realise the given expression using only NAND gates and inverters : $xyz + x'y'z'$. (4)
- ii) Design a full adder, construct the truth table, simplify the output equations and draw the logic diagram. (8)

(OR)



- b) i) 1) Draw the logic diagram for a four bit parallel input parallel output register. Indicate inputs, outputs and a negative edge triggered clock. **(4)**
2) Draw a simple ring counter and briefly describe its counting action. **(4)**
 - ii) 1) Give a brief explanation of an A/D conversion and the need for the A/D conversions. **(4)**
2) Convert 95.0625_{10} to binary. **(4)**
 - 15. a) i) Draw a typical television video signal. Explain how this is converted to an image on a TV screen. **(6)**
ii) What is the need for modulation? Explain the principles behind amplitude modulation and frequency modulation. Compare and contrast the two types of modulation. **(10)**
- (OR)
- b) i) With neat diagrams explain any one method of amplitude modulation and its corresponding demodulation. **(8)**
 - ii) Write short notes on the following modes of communication :
 - 1) Microwave **(4)**
 - 2) Optical fiber. **(4)**
-