

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 31566**

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2013.

Fourth Semester

Mechanical Engineering

ME 2255/ME 46/ EC 1265/10122 ME 406/080120019 — ELECTRONICS AND MICROPROCESSORS

(Common to Automobile Engineering, Production Engineering and Mechanical and Automation Engineering)

(Regulation 2008/2010)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Sketch neatly the energy band diagram for Conductors, Semi Conductors and Insulators.
2. Differentiate P and N type materials.
3. Sketch the characteristics of UJT.
4. State any two applications of SCR.
5. Convert the decimal number 148 into a hexadecimal number.
6. Design a AND gate using a NAND gate.
7. List the various addressing modes of 8085.
8. Differentiate RAM and ROM.
9. What are the criterion to be considered for interfacing a microprocessor?
10. List the fundamental I/O techniques.

PART B — (5 × 16 = 80 marks)

11. (a) Write short notes on :
- (i) Intrinsic semiconductors
  - (ii) Extrinsic semiconductors
  - (iii) P type material
  - (iv) N type material. (16)

Or

- (b) (i) Explain how zener diode is used as a voltage regulator. (10)
- (ii) Discuss the characteristics of zener diode. (6)
12. (a) (i) Explain about the operation of a CE amplifier. (8)
- (ii) Explain about the operation of a Class A amplifier. (8)

Or

- (b) (i) Explain about the operation and characteristics of SCR. (8)
- (ii) Explain about the operation and characteristics of TRIAC. (8)
13. (a) Design a full adder and a full subtractor. (16)

Or

- (b) (i) Explain the operation of a 3-bit binary counter circuit. (8)
- (ii) Explain the basic concept of Analog to Digital conversion. (8)
14. (a) Briefly discuss about architecture of 8085. (16)

Or

- (b) Discuss all the Data transfer, Arithmetic and Logical Instructions. (16)
15. (a) (i) Compare the memory mapped I / O and Peripheral I / O. (8)
- (ii) Write short notes on Output interfacing. (8)

Or

- (b) Explain the 8085 based temperature control system. (16)