



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 52844**

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2017

Third/Fourth Semester

Automobile Engineering

ME 2255 – ELECTRONICS AND MICROPROCESSORS

(Common to Mechanical Engineering/Mechanical and Automation Engineering/  
Production Engineering)

(Regulations 2008)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A

(10×2=20 Marks)

1. Define doping.
2. What is p-type semiconductor ?
3. What is the importance transistor biasing ?
4. Draw the V-I characteristic of Triac.
5. State De Morgan's theorem.
6. Reduce  $A'B'C' + A'BC' + A'BC$ .
7. Write about the sign flag of 8085.
8. What is the addressing mode of the instruction - MOV A, M ?
9. Explain IN and OUT instruction of 8085.
10. List some application of microprocessor 8085.

PART – B

(5×16=80 Marks)

11. a) i) Explain the V-I characteristics of PN diode with neat diagram. (8)  
ii) Explain the V-I characteristics of zener diode with neat diagram. (8)

(OR)

- b) Explain the half wave, full wave and bridge full wave rectifier circuit with necessary diagram. (16)



12. a) Explain the construction, working and volt-ampere characteristics of UJT. (16)  
(OR)
- b) Explain the Common Emitter and Common Base configuration and derive the relation between  $\alpha$  and  $\beta$ . (16)
13. a) Design a 3-bit Asynchronous Binary Counter using JK flip flop. (16)  
(OR)
- b) Explain with necessary diagram the four basic shift registers. (16)
14. a) Explain the architecture of 8085 with neat diagram. (16)  
(OR)
- b) Explain the pin configuration of 8085 with pin diagram. (16)
15. a) Explain the interfacing diagram of 8085 with stepper motor, with assembly language code. (16)  
(OR)
- b) Design a microprocessor system to control traffic lights. (16)
-