



Reg. No. :

|  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code : X 20389**

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2020  
Second Semester

Computer Science and Engineering  
CS 6201 – DIGITAL PRINCIPLES AND SYSTEM DESIGN  
(Common to Information Technology)  
(Regulations 2013)

(Common to PTCS 6201 – Digital Principles and System Design for B.E.  
(Part-Time) – Computer Science and Engineering – First Semester (Regulations 2014))

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

**(10×2=20 Marks)**

1. Convert  $(126)_{10}$  to octal number and binary number.
2. Write short notes on weighted binary codes.
3. Implement a full adder with  $4 \times 1$  Multiplexer.
4. Write the Data flow description of a 4-bit Comparator.
5. State the excitation table of JK-Flip Flop.
6. A seven bit Hamming code is received as 1111110. What is the correct code ?
7. When do race conditions occur ?
8. Define merger graph.
9. List the major differences between PLA and PAL.
10. What is memory decoding ?

PART – B

**(5×16=80 Marks)**


11. a) Simplify the following Boolean expression in
  - i) Sum-of-product
  - ii) Product-of-sum using Karnaugh map
$$AC' + B'D + A'CD + ABCD$$

**(16)**

(OR)



 - b) i) Express the following function in sum of min-terms and product of max-terms :  
 $F(x, y, z) = x + yz.$  (8)
- ii) Convert the following logic system into NAND gates only. (8)



12. a) Design a full adder with inputs x, y, z and two outputs S and C. The circuit performs  $x + y + z$ , z is the input carry, C is the output carry and S is the sum. (16)
- (OR)
- b) Design a logic circuit that accepts a 4-bit Grey Code and convert it into 4-bit binary code. (16)
13. a) Design a sequence detector that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line and produces an output whenever this sequence is detected. (16)
- (OR)
- b) Design a three bit synchronous counter with T flip flop and draw the diagram. (16)
14. a) Explain the analysis and design procedures of synchronous sequential circuits. (16)
- (OR)
- b) With necessary example and diagram, explain the concept of reduction of state and flow tables. (16)
15. a) Design a 16 bit RAM array ( $4 \times 4$  RAM) and explain the operation. (16)
- (OR)
- b) Explain the following :  
 i) ASIC (8)  
 ii) Field Programmable Gate Array. (8)