

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51376

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2016

Third Semester

Computer Science and Engineering

**CS 2202/CS 34/EC 1206 A/080230012/10144 CS 303 – DIGITAL PRINCIPLES AND
SYSTEM DESIGN**

(Common to Information Technology)

(Regulations 2008/2010)

(Common to PTCS 2202 – Digital Principles and System Design for B.E. (Part-Time)

Second Semester – CSE – Regulations 2009)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A (10 × 2 = 20 Marks)

1. Convert the gray code (11011) to binary code.
2. Simplify the following expression with Boolean laws :
 $Y = ABC + AB'C + ABC'$
3. Implement a full adder with two half adders.
4. Implement a 4-bit even parity checker.
5. Write the HDL data flow description of four bit adder.
6. Differentiate between encoder and decoder.
7. Realize a JK flip-flop using D flip-flop.
8. Write the HDL code for up-down counter using behavioural model.
9. What is primitive flow table ?
10. What are static '1' and static '0' hazards ?

PART - B (5 × 16 = 80 Marks)

11. (a) (i) List the ASCII code for the 10 decimal digits with an odd parity in the leftmost position. (6)
- (ii) Simplify the three variable logic expression. (6)
- $Y = \pi M(1, 3, 5)$
- (iii) Implement $Y = (A'B + AB')(C + D')$ using NOR gates. (4)

OR

- (b) Simplify the following Boolean function by using tabulation method : (16)
- $F(A, B, C, D) = \Sigma(1, 4, 6, 7, 8, 9, 10, 11, 15)$

12. (a) (i) Analyse the combinational circuit shown in figure 12 (a) (i) to determine the truth table and the Boolean expressions governing the *outputs of the circuit*. (10)

 


Figure 12 (a) (i)

- (ii) Explain BCD adder with a neat block diagram. (6)

OR

- (b) (i) Design a BCD to excess-3 code converter using logic gates. (12)
- (ii) Draw the diagram of a 4-bit adder subtracter using full adders. (4)

13. (a) (i) Realize 4×16 decoder using two 3×8 decoders with enable input. (4)
- (ii) Implement the two following Boolean functions using 8×2 PROM. (6)
- $F1 = \Sigma m(3, 5, 6, 7)$ and $F2 = \Sigma m(1, 2, 3, 4)$.
- (iii) Implement the following function using a multiplexer. (6)
- $F(W, X, Y, Z) = \Sigma m(0, 1, 3, 4, 8, 9, 15)$.

OR

- (b) Implement the following two Boolean functions using PLA with 3 inputs, 4 product terms and 2 outputs.

$$F1 = \Sigma m(3, 5, 6, 7) \text{ and } F2 = \Sigma m(1, 2, 3, 4). \quad (16)$$

14. (a) Design a sequential circuit with two T flip-flops A and B, one input X and one output Z is specified by the following next state and output equation is

$$A(t + 1) = BX' + B'X$$

$$B(t + 1) = AB + BX + AX$$

$$Z = AX' + A'B'X$$

- (i) Draw the logic diagram of the circuit
(ii) List the state table for the sequential circuit.
(iii) Draw the corresponding state diagram. (16)

OR

- (b) (i) Draw and explain the parallel in serial out shift register and explain. (8)
(ii) Draw the block diagram of Johnson counter and explain. (8)

15. (a) (i) Explain the types of hazards in digital circuits.
(ii) Implement the switching function $F = \Sigma m(1, 3, 5, 7, 8, 9, 14, 15)$ by a static hazard free 2 level AND-OR gate network.

OR

- (b) Explain the steps for the design of asynchronous sequential circuits.
-