

**ANNA UNIVERSITY COIMBATORE**  
**B.E. / B.Tech. DEGREE EXAMINATION – DECEMBER 2008**  
**THIRD SEMESTER - CSE / IT**  
**IT301- DIGITAL PRINCIPLES AND SYSTEM DESIGN**

**Time: Three Hours**

**Maximum: 100 Marks**

**PART A – (20 x 2 = 40 Marks)**

**Answer ALL Questions**

1. Solve  $(247.36)_8 = (x)_2 = (y)_{16}$
2. Find the complement of  $F = x(y + z)$  and show that  $F + F' = 1$ .
3. Realize the function  $Y = A + B$  using only NAND gate.
4. Express the minterm  $m_{21}$  using minimum number of variables.
5. Implement a full adder using two half adder & OR gate
6. Mention the need for a carry look ahead adder.
7. State the condition to check the equality of two n bit binary numbers A and B.
8. What are the applications of HDL processing?
9. Realize the following expressions using verilog HDL.

$$X = A + B'C + BD$$

$$Y = (A + B)(C' + D)$$

10. Draw the logic diagram of a combinational circuit which helps in data distribution.
11. Realize the function  $F(A, B, C) = \sum m(1, 2, 6, 7)$  using a decoder.
12. What are the different types of programming the PLA?
13. Construct JK flipflop using D flipflops ?
14. Compare combinational circuit and sequential logic circuit
15. Write the HDL behavioural description of 4 bit shift registers
16. What is a race around condition?

17. Draw the hazard free circuit for the Boolean Expression

$$y = x_1x_2 + \overline{x_2}x_3$$

18. Define the fundamental mode.
19. What are the steps to be followed for the purpose of merging a flow table?
20. What is the reason for essential hazard?

**PART B – (5 x 12 = 60 Marks)**

**Answer Any FIVE Questions**

21. (a) Simplify using K-map and express the reduced expression in SOP and POS form.

$$F = \sum m(0, 6, 8, 13, 14) + \sum d(2, 4, 10) \quad (8)$$

- (b) Reduce the following Boolean expression

$$F = (x'y' + z)' + z + xy + wz \quad (4)$$

22. Solve the given Boolean function using Quine MC Cluskey method and draw the logic diagram for the reduced expression using only NOR gates.

$$F(A, B, C, D) = \sum m(1, 3, 5, 7, 9, 15) + \sum d(4, 6, 12, 13) \quad (12)$$

23. Design a code converter that converts a decimal digit from the 8, 4, -2, -1 code to BCD. (12)
24. (a) Write down the behavioral description of a 4 to 1 line Multiplexer. (4)


(b) Implement the following two Boolean functions using a PLA.

$$A(x, y, z) = \sum m(1, 2, 4, 6)$$

$$B(x, y, z) = \sum m(0, 1, 2, 6) \quad (8)$$

25. Design a parallel counter which counts the sequence 0, 1, 2, 5, 6, 7 using JK flipflops. (12)

 26. Design a sequential circuit specified by the given state diagram of a sequence detector using 'D' flip flops. (12)



27. Explain the different types of hazards in combinational circuits and Sequential circuits with an example. (12)

28. (a) Obtain a primitive flow table for an asynchronous sequential circuit with 2 inputs x, y and output Q. The output Q = x as long as y = 1 and retains this value after y goes to 0. Once y goes to 0, a change in x does not change the value of output Q. (8)

(b) Assign output values to don't cares in the flow table to avoid transient output pulses. (4)

	00	01	11	10
a	a,0	b,-	-, -	d,-
b	a,-	b,1	b,1	c,-
c	b,-	-, -	b,-	c,0
d	c,-	d,1	c,-	d,1

\*\*\*\*\*THE END\*\*\*\*\*