

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51401

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2014.

Fourth Semester

Electronics and Communication Engineering

EC 2254/EC 44/EC 1254/080290022/10144 EC 405 – LINEAR INTEGRATED
CIRCUITS

(Regulation 2008/2010)

(Common to PTEC 2254 Linear Integrated Circuits for B.E. (Part-Time)–
Third Semester ECE – Regulation 2009)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. List any two advantages of ICS over discrete components.
2. Define Slew rate.
3. What is a voltage follower?
4. Draw the circuit diagram of peak detector.
5. State the operation of a basic PLL.
6. What is the need for frequency synthesizer?
7. What is a sample/hold circuit?
8. Give any two advantages of SA type ADC.
9. List the types of multivibrators.
10. What is an opto-coupler?

PART B — (5 × 16 = 80 marks)

11. (a) Explain the construction of monolithic bipolar transistor, monolithic diode and integrated resistors. (16)

Or

- (b) Explain the Internal circuit diagram of IC 741. Discuss its AC and DC performance characteristics. (16)

12. (a) With neat diagram explain logarithmic amplifier and antilogarithmic amplifier. (16)

Or

- (b) With neat diagram explain the application of op-amp as precision rectifier, clipper and clamper. (16)

13. (a) Explain the working of Analog multiplier using emitter coupled transistor pair. Discuss the applications of analog multiplier IC. (16)

Or

- (b) Explain the application of PLL as AM detection, FM detection and FSK demodulation. (16)

14. (a) Explain weighted resistor type and R-2R Ladder type DAC. (16)

Or

- (b) Explain Flash type, Single slope type and Dual slope type ADC. (16)

15. (a) With neat diagram explain IC 723 General Purpose regulator. (16)

Or

- (b) Explain in detail voltage to frequency and frequency to voltage converters. (16)