



Reg. No. :

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Question Paper Code : 52450

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2017

Fifth Semester

Electronics and Communication Engineering

EC2305 – TRANSMISSION LINES AND WAVE GUIDES

(Regulations 2008)

[Common to PTEC2305 – Transmission Lines and Wave guides for BE

(Part – Time) Fourth Semester – ECE – Regulations 2009]

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What are the secondary constants of a line ?
2. What are called constant-k filters ?
3. What is the condition for a distortion less line ?
4. Draw the input impedance pattern for a lossless line when short circuited.
5. What is the relationship between standing wave ratio and reflection coefficient ?
6. What are the assumptions for the analysis of radio frequency line ?
7. What are the dominant modes for TE and TM waves in parallel plane wave guide ?
8. Write the expression for cutoff wavelength of the wave which is propagated in between two parallel planes.
9. Define – Phase Velocity and Group Velocity.
10. What are the characteristics of TEM waves ?

PART – B

(5×16=80 Marks)

11. a) Sketch the reactance curve of a constant-K low pass filter. Determine attenuation constant and phase constant in pass band and stop band plot it. (16)

(OR)

- b) Design a m-derived low pass filter (T and π section) having a design resistance of $R_0 = 500 \Omega$ and the cut off frequency (f_c) of 1500 Hz and an infinite attenuation frequency (f_∞) of 2000 Hz. (16)



12. a) Derive the general transmission line equations (with necessary diagrams) for voltage and current at any point on a line. (16)
- (OR)
- b) A generator of 1V, 1000 Hz supplies power to 1000Km long open wire line terminated in its characteristic impedance Z_0 and having the following parameters. $R = 15 \Omega$, $L = 0.004 \text{ H}$, $C = 0.008 \mu \text{ F}$, $G = 0.5 \mu \text{ mhos}$. Calculate the characteristic impedance, propagation constant and the phase velocity. (16)
13. a) Antenna with impedance $40 + j30 \Omega$ is to be matched to a 100Ω lossless line with a shorted stub. Determine the required stub admittance, distance between the stub, stub length and standing wave ratio on each ratio of the system using Smith chart. (16)
- (OR)
- b) A lossless transmission line with characteristic impedance $Z_0 = 300 \Omega$ is connected to a load $Z_L = 120 - j60 \Omega$. Calculate input impedance (Z_{in}), standing wave ratio, Γ (Reflection coefficient) and input current. Given, length of the transmission line = 2 m, phase velocity (v_p) = $2.5 \times 10^8 \text{ m/s}$, operating frequency (f) = 100 MHz, source impedance (Z_s) = 300Ω and source voltage (V_s) = 60V. (16)
14. a) Obtain the field equations of Transverse Electric waves in parallel planes. (16)
- (OR)
- b) i) Design a symmetrical bridge T attenuator with an attenuation of 40 dB and impedance of 600Ω . (10)
- ii) Differentiate between attenuator and amplifier. List the practical applications of attenuators. (6)
15. a) Derive the field equations of Transverse Electric waves travelling in Z direction in a rectangular wave guide. (16)
- (OR)
- b) Derive the resonant frequency of a rectangular resonator. (16)