



Reg. No. :

| | | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

Question Paper Code : 91453

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019

Fifth Semester

Electronics and Communication Engineering

EC 6503 – TRANSMISSION LINES AND WAVE GUIDES

(Regulations 2013)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What are the primary and secondary constants of a transmission line ?
2. What is a distortionless line ? What is the condition for a distortionless line ?
3. Define insertion loss.
4. A transmission line has $Z_0 = 745 \angle 12^\circ$ and is terminated as $Z_R = 100 \Omega$. Calculate the reflection loss in dB.
5. Write down the expression to determine the length of the stub.
6. What is the application of quarter wave line matching section ?
7. What are called crystal filters ?
8. Design a low pass filter T section having cut off frequency of 2 KHz to operate with a terminated load resistance of 500Ω .
9. What is TEM wave or principal wave ?
10. An air filled resonant cavity with dimensions $a = 5$ cm, $b = 4$ cm and $c = 10$ cm is made of copper. Find the resonant frequency of lowest order mode.



11. a) A generator of 1V, 1000 Hz supplies power to a 100 km open wireline terminated in Z_0 and having the following parameters. $R = 10.4 \text{ ohm/km}$, $G = 0.8 \times 10^{-6} \text{ mho/km}$, $L = 0.00367 \text{ henry/km}$ and $C = 0.00835 \text{ } \mu\text{F/km}$. Calculate Z_0 , α , λ , β , v . (13)

(OR)

- b) The characteristic impedance of a uniform transmission line is $2000 \text{ } \Omega$ at a frequency of 1000 Hz. At this frequency the propagation constant was found to be $0.054 \angle 60^\circ$. Determine the values of line constants. (13)

12. a) Explain the parameters of open-wire and co-axial lines at radio frequency. (7+6=13)

(OR)

- b) The terminating load of UHF transmission line working at 300 MHz is $(50 + j50) \text{ } \Omega$. Calculate VSWR and the position of the voltage minimum nearest to the load if the characteristic impedance of the line is $50 \text{ } \Omega$. (13)

13. a) Explain the technique of single stub matching and discuss operation of quarter wave transformer. (13)

(OR)

- b) A single stub is to match a $400 \text{ } \Omega$ line to a load of $(200 - j100) \text{ } \Omega$. The wavelength is 3m. Determine the position and length of the short circuited stub. (13)

14. a) Derive the relevant equations of m derived low pass filter and design a m derived T type low pass filter to work into the load of $600 \text{ } \Omega$ and cut off frequency at 5 KHz and peak attenuation at $1.25f_c$. (6+7)

(OR)

- b) Explain the structure and application of crystal filter. A π section filter network consists of a series arm inductance of 20 mH and two shunt capacitor of $0.16 \text{ } \mu\text{F}$ each. Calculate the cut off frequency, attenuation and phase shift at 15 kHz. What is the value of nominal impedance in the pass band? (3+3+3+4=13)



15. a) For a frequency of 10 GHz and plane separation of 5 cm in air, find the cut off frequency, cut off wavelength, phase velocity and group velocity of the wave. (13)

(OR)

- b) Derive the expressions for TE and TM mode in rectangular wave guide. (13)

16. a) A TE₁₀ wave at 10 GHz propagates in a brass $\sigma_c = 1.57 \times 10^7 \text{ (S/m)}$ rectangular waveguide with inner dimensions $a = 1.5 \text{ cm}$ and $b = 0.6 \text{ cm}$, which is filled with $\epsilon_r = 2.25$, $\mu_r = 1$, loss tangent = 4×10^{-4} . Determine :

- 1) the phase constant,
- 2) the guide wavelength,
- 3) the phase velocity,
- 4) the wave impedance,
- 5) the attenuation constant due to loss in the dielectric and,
- 6) the attenuation constant due to loss in the guide walls. (15)

(OR)

- b) i) Discuss in detail about the variation of input impedance along open and short circuited lines with relevant graphs. (10)

- ii) A lossless line has a standing wave ratio of 4. The R_0 is $150 \text{ } \Omega$ and the maximum voltage measured in the line is 135V. Find the power delivered to the load. (5)