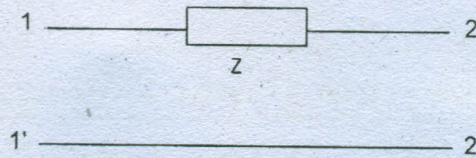
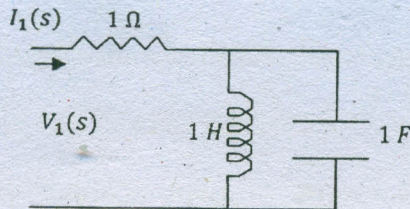


5. Find the z and y parameters if they exist for the two-port network shown below.



6. Find the driving point admittance function for the network shown.



7. Define cut-off frequency and image impedance of a filter network.
 8. What is constant k filter? Why it is called prototype filter section?
 9. Test whether the polynomial $P(s) = s^4 + 3s^2 + 2s + 12$ is Hurwitz.
 10. Where will be the location of poles and zeros of an LC immittance function?

PART B — (5 × 16 = 80 marks)

11. (a) (i) In the circuit of Fig. 1, the switch has been in position 1 for sufficient time to establish steady-state conditions. The switch is then moved to position 2. Find the current transient and the energy dissipated in the resistors during the transient. (10)

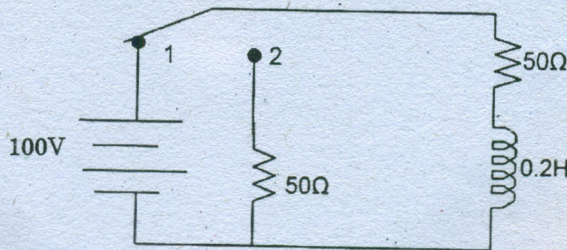


Fig.1

- (ii) A transient that increases from zero toward a positive steady-state magnitude is 49.5 at $t_1 = 5.0ms$ and 120 at $t_2 = 20.0ms$. Obtain the time constant τ . (6)

Or

- (b) (i) A series RC circuit with $R = 100\ \Omega$ and $C = 25\ \mu F$ has sinusoidal voltage $200 \sin 500t$ applied at $t = 0$. Find the expression for current. The initial charge on capacitor is zero. (8)
- (ii) A series RLC circuit with $R = 100\ \Omega$, $C = 100\ \mu F$ and $L = 0.1 H$ has a constant voltage $200\ V$ applied at $t = 0$. Find the current transient, assuming zero initial charge on the capacitor. (8)
12. (a) Find poles and zeros of $H(s) = 10/(s^2 + 2s + 26)$. Place them in the s-domain and use the pole-zero plot to sketch $H(i\omega)$. (16)

Or

- (b) Find the Fourier series for the waveform shown in Fig. 2. (16)

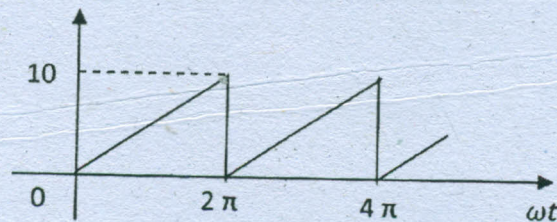


Fig.2

13. (a) (i) Determine the open-circuit impedance parameters of the two-port network shown in Fig.3. (10)

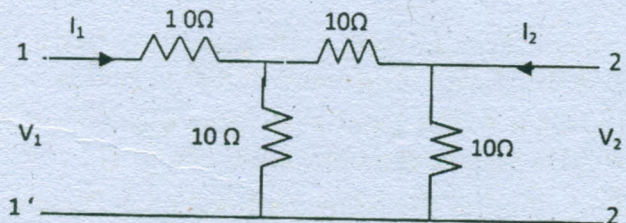


Fig.3

- (ii) The two currents of a two-port network are

$$I_1 = 2V_1 - V_2$$

$$I_2 = -V_1 + 4V_2$$

What is the equivalent π -network? (6)

Or

- (b) (i) The following equation gives the voltage and current at the input port of a two-port network. Determine the transmission parameters. (6)

$$V_1 = 5V_2 - 3I_2$$

$$I_1 = 6V_2 - 2I_2$$

- (ii) Determine the image parameters of the T network shown in Fig. 4. (10)

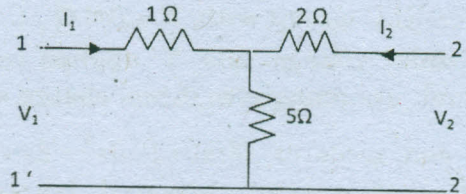


Fig.4

14. (a) (i) Obtain the characteristic impedance of the symmetrical T network shown in Fig. 5. (8)

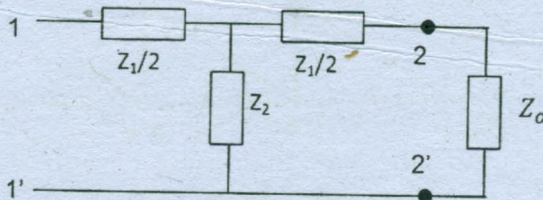


Fig.5

- (ii) Design a constant k low pass filter with a cut-off frequency of 1 kHz, and design impedance of 500 Ω . (8)

Or

- (b) (i) Design a m -derived high pass filter with a cut-off frequency of 10 kHz, design impedance of 600 Ω and $m = 0.3$. (8)
(ii) Design a k -type band pass filter with cut-off frequencies 1 kHz and 10 kHz and design impedance of 500 Ω . (8)
15. (a) (i) Test whether the following function is Positive real. (6)

$$Z(s) = \frac{s^2 + 2s + 25}{(s + 4)}$$

- (ii) Synthesize the following RC impedance function in Foster forms. (10)

$$Z(s) = \frac{2(s+2)(s+4)}{(s+1)(s+3)}$$

Or

- (b) (i) Synthesize the following LC impedance function in Cauer II form. (8)

$$Z(s) = \frac{s^3 + 2s}{s^4 + 4s^2 + 3}$$

- (ii) Synthesize the following RL impedance function in Cauer I form. (8)

$$Z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$$