

TIME : 3 Hours


Max.Marks : 100

PART – A

(20 x 2 = 40 MARKS)

ANSWER ALL QUESTIONS

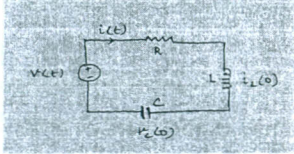1. What do we mean by Network synthesis? How is it different from network analysis?
2. Transform the series RLC network shown, to a network in the Laplace domain



3. Compare natural and forced response in a circuit
4. Find the Laplace transforms of the function: (i) $\sin 3t$, (ii) $t \sin 2t$
5. List the fundamental difference between an RC and an LC impedance function
6. Define resonance frequency and quality factor for an RLC network.
7. Define poles and zeros in a network function.
8. Write the Fourier transform $F(j\omega)$ of an even function $f(t)$
9. List four important properties of a driving point impedance function of an RC network.
10. In terms of ABCD parameters when is a two-port network symmetrical?


11. Show how you can connect two 2-port networks in parallel
12. What is meant by impedance matching?
13. Draw the ideal characteristics of low pass and high pass filters.
14. Discuss the merits of m-derived filters.
15. Design a high pass filter with a cut-off frequency of 1 KHz with a terminated design impedance of 800 ohms.
16. What are the conditions for characteristic impedances in the pass and stop bands?
17. Define propagation constant for a network
18. Test whether the polynomial $P(s) = s^4 + s^3 + s^2 + 2s + 2$ is Hurwitz.
19. What are the properties of a positive real function?
20. State the properties of RC driving point impedance function.

PART - B

(5 x 12 = 60 MARKS)

ANSWER ANY FIVE QUESTIONS

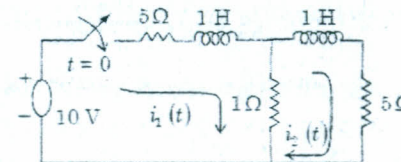21. For the network shown in Figure, find the current $i_2(t)$. The Network is deenergised before $t = 0$.



22. Derive the expression for RLC transient circuit and state its different conditions

23. Draw the pole zero diagram for the given network function and hence obtain $v(t)$

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)}$$

24. Derive expressions for evaluating the driving point impedance at the output port of a network having a source impedance Z_S at the input, in terms of


(i) Z-parameters of the network, and

6

(ii) Y-parameters of the network.

6

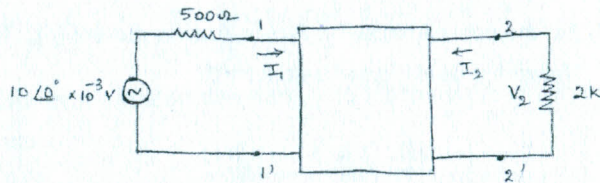25. The hybrid parameters of a two port network shown in Fig are $h_{11} = 1 K$; $h_{12} = 0.003$; $h_{21} = 100$; $h_{22} = 50 \mu V$. Find V_2 and Z-parameters of the network.



26. Design an M-derived low pass filter (T and p-section) to match a line having characteristic impedance of 500ohms and to pass signals up to 1 KHz with infinite

attenuation occurring at 1.2 KHz

27. Realize the function $z(s)$ in Foster I and Foster II

$$z(s) = \frac{5s(s^2+4)}{(s^2+1)(s^2+3)}$$

28. Determine if the following function are positive real. Give reasons to justify your conclusions.

$$\frac{4(s^2+1)(s^2+16)}{s(s^2+4)}$$

$$\frac{(s+3)(s+7)}{(s+2)(s+4)}$$

-----XXXXX-----