

20/6/16

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 83074

M.E. DEGREE EXAMINATION, MAY/JUNE 2016

Second Semester

Applied Electronics

AP 7201 – ANALYSIS AND DESIGN OF ANALOG INTEGRATED CIRCUITS

(Common to M.E. VLSI Design)

(Regulations 2013)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A (10 × 2 = 20 Marks)

1. Draw the circuit diagram of a source follower with a resistive load using N-channel MOSFETS.
2. Draw the small-signal equivalent circuit of the common gate stage.
3. State Miller effect.
4. Define Noise Bandwidth.
5. Draw a single stage amplifier with voltage shunt feedback.
6. Define slew rate.
7. Mention the different methods of Op-amp compensation techniques.
8. Define Gain margin (G_m) and Phase margin (P_m)
9. Derive for PTAT voltage with circuit diagram.
10. Draw a simple current mirror and write the expression for output current.

PART – B (5 × 16 = 80 Marks)

11. (a) Draw a MOS Differential amplifier with active load and derive for A_d and A_c . (16)

OR

- (b) (i) Explain the common-source amplifier with source degeneration and derive its transconductance (G_m) and output resistance (R_o) (10)
(ii) Draw a cascade current source and derive its output impedance with equivalent circuit. (6)
12. (a) (i) Explain the statistical characteristic of Noise in single stage amplifier. (8)
(ii) Calculate the transfer function for a source follower with $C_{gs} = 7.33$ pF, $C_{gd} = 0.1$ pF, $C_{gb} = 0.05$ pF, $C_{sb} = 0.5$ pF, $k'W/L = 100$ mA/V², $R_L = 2$ k Ω , $R_S = 190$ k Ω and $I_D = 4$ mA. Ignore the body effect, Assume $G_m = 28.2$ mA/V, $C'_{gd} = 0.15$ pF. (8)

OR

- (b) Derive for pole-zero frequencies of common gate stage with ideal current source as active load. (16)
13. (a) (i) Draw the basic amplifier without feedback and derive for its transfer gain using feedback concept and also write the expression for A_{VF} (8)
(ii) Explain the concept of gain boosting with an example. (8)

OR

- (b) (i) Explain the methods of improving slew rate of op-amp. (8)
(ii) Draw a one stage op-amp and give the circuit description. Also write the expression for open loop gain. (8)
14. (a) Draw two stage op-amp with miller's compensating capacitor with the equivalent circuit. Derive for its pole and zero frequencies. (16)

OR

- (b) Discuss about multi-pole systems for stability in Phase margin. (16)
15. (a) (i) Explain constant G_M biasing circuit. (8)
(ii) Draw a temperature independent biasing circuits using zener diode and derive its temperature co-efficient. (8)

OR

- (b) (i) Draw and explain cascade current mirror and derive for output current and output resistance. (10)
(ii) Describe the logical steps to build a Band gap reference voltage source. (6)