



PART B — (5 × 16 = 80 marks)

11. (a) (i) Find the current  $I$  and voltage across  $30\Omega$  of the circuit shown in Fig.11 (a) (i). (8)

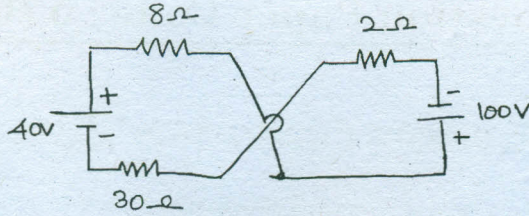


Fig. 11 (a) (i)

- (ii) Determine, the current in all the resistors of the circuit shown in Fig. 11 (a) (ii) (8)

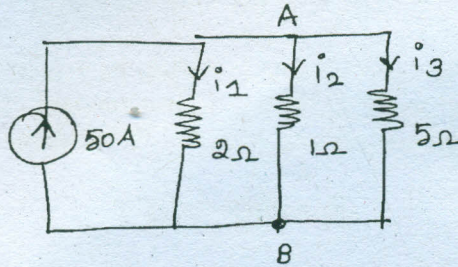


Fig. 11 (a) (ii)

Or

- (b) (i) Determine the current through each resistor in the circuit shown in Fig 11 (b) (i). (6)

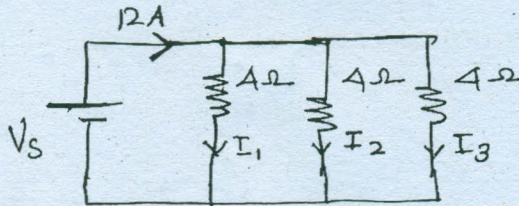


Fig 11 (b) (i)

- (ii) When a dc voltage is applied to a capacitor, voltage across its terminals is found to build up in accordance with  $v_c = 50(1 - e^{-100t})$ . After 0.01 S the current flow is equal to 2 mA.

- (1) Find the value of capacitance in farad.
- (2) How much energy stored in the electric field? (10)

12. (a) (i) Determine the current in the  $5\Omega$  resistor in the network shown in Fig. 12 (a) (i). (8)

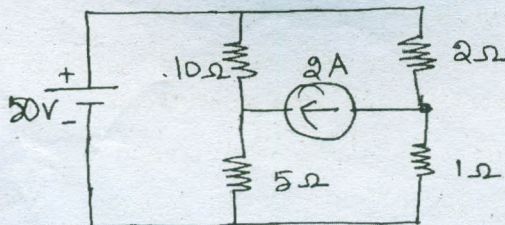


Fig. 12 (a) (i)

- (ii) Find out the current in each branch of the circuit shown in Fig. 12 (a) (ii). (8)

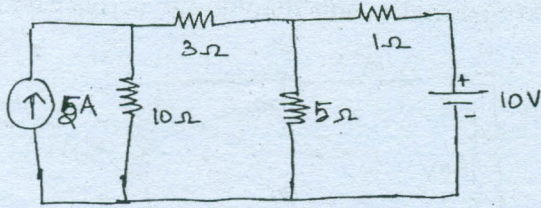


Fig. 12 (a) (ii)

Or

- (b) (i) Determine current in each mesh of the circuit shown in Fig. 12 (b) (i). (8)

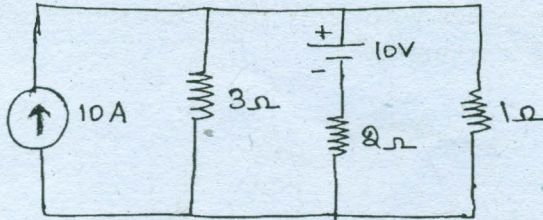


Fig. 12 (b) (i)

- (ii) Determine the voltages at each node of the circuit shown in Fig. 12 (b) (ii). (8)

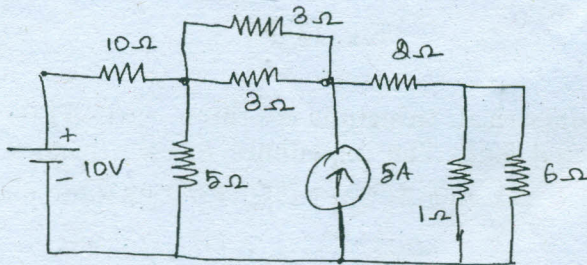


Fig. 12 (b) (ii)

13. (a) For the circuit shown in Fig. 13 (a), determine the impedance at resonant frequency, 10Hz above resonant frequency, and 10Hz below resonant frequency. (16)

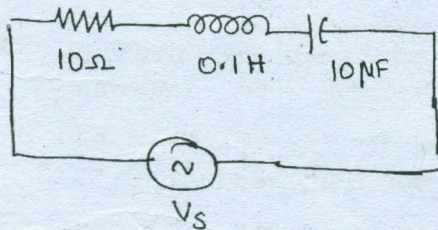


Fig. 13 (a)

Or

- (b) Explain that how to derive Q factor of parallel resonance. (16)

14. (a) A series RL circuit with  $R = 30\Omega$  and  $L = 15H$  has a constant voltage  $V = 60V$  applied at  $t = 0$  as shown in Fig. 14 (a). Determine the current  $i$ , the voltage across resistor and the voltage across the inductor. (16)

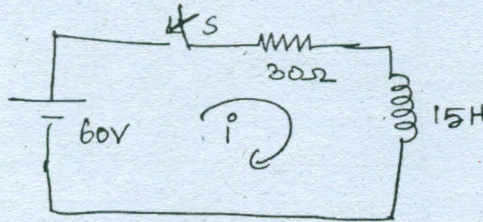


Fig. 14 (a)

Or

- (b) The circuit shown in Fig. 14 (b) consists of resistance, inductance and capacitance in series with 100V DC when the switch is closed at  $t = 0$ . Find the current transient. (16)

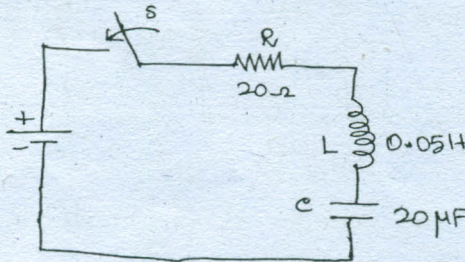


Fig. 14 (b)

15. (a) (i) A symmetrical three-phase; three wire 440V supply to a star connected load. The impedance in each branch are  $Z_R = 2 + j3\Omega$ ,  $Z_Y = 1 - j2\Omega$  and  $Z_B = 3 + j4\Omega$ . Find its equivalent delta connected load. (8)
- (ii) A three phase, balanced delta-connected load of  $4 + j8\Omega$  is connected across a 400V,  $3\phi$  balanced supply. Determine the phase currents and line currents. (Phase sequence is RYB). (8)

Or

- (b) (i) A symmetrical three-phase, three wire 400V, supply is connected to a delta-connected load. Impedances in each branch are  $Z_{RY} = 10\angle 30^\circ \Omega$ ,  $Z_{YB} = 10\angle 45^\circ \Omega$  and  $Z_{BR} = 2.5\angle 60^\circ \Omega$ . Find its equivalent star-connected load. (8)
- (ii) A balanced star connected load having an impedance  $15 + j20\Omega$  per phase is connected to  $3\phi$ , 440V, 50HZ. Find the line current and power absorbed by the load. (8)