



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : X 60492

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2020

Second Semester

Electrical and Electronics Engineering

EE 2151/EE 25/EE 1151/080280005/10133 EE 205 – CIRCUIT THEORY

(Common to Electronics and Instrumentation Engineering/Instrumentation and Control Engineering)

(Regulations 2008/2010)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. State Ohm's law.
2. State Kirchhoff's laws.
3. Write the objective of star delta transformation.
4. Define Reciprocity theorem.
5. A series resonant circuit has a bandwidth of 20 kHz and a quality factor of 40. The resistor value is 10 k Ω . Find the value of L of this circuit.
6. Define mutual inductance.
7. Find the time constant of RL circuit having $R = 10 \Omega$ and $L = 0.1 \text{ mH}$.
8. A RLC series circuit has $R = 10 \Omega$. $L = 2 \text{ H}$. What value of capacitance will make the circuit critically damped ?
9. What are the advantages of three phase system ?
10. Define line voltage and line current.



PART – B

(5×16=80 Marks)

11. a) In the circuits of Fig. 1, find the current I by the mesh method. (16)

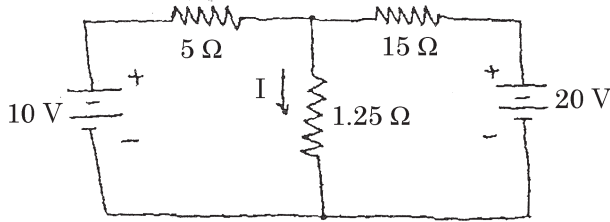


Fig. 1

(OR)

b) Write the nodal equations for the network of Fig. 2. Hence find the potential difference between nodes 2 and 4.


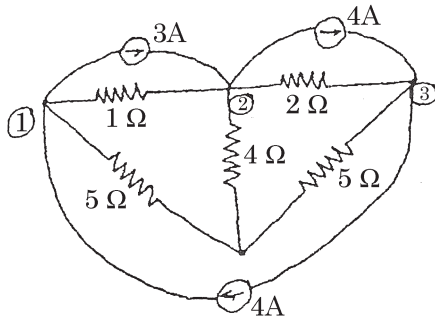



Fig. 2

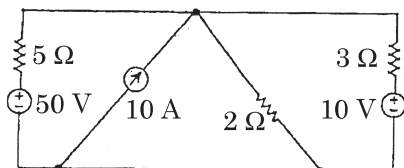12. a) i) Using source transformation, replace the current source in the circuit shown below by a voltage source and find the current delivered by the 50 V voltage source. (8)






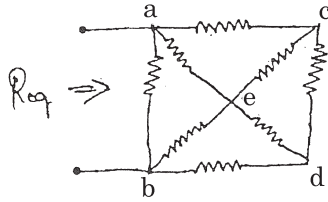- ii) Calculate the equivalent resistance R_{ab} when all the resistance values are equal to 1Ω for the circuit shown below. (8)




(OR)

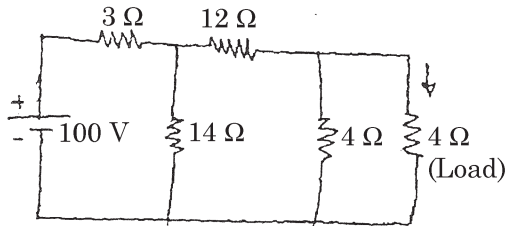- b) i) Verify Reciprocity theorem for the circuit shown below. (8)



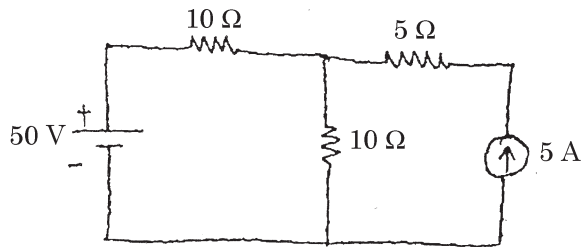- ii) Find the current through various branches of the circuit shown below, by employing superposition theorem. (8)



13. a) Obtain the expression for voltage, current and frequency in a series resonant circuit and draw its frequency response curve. (16)

(OR)

- b) Explain the single tuned circuit and obtain expression for maximum amplification. (16)



14. a) Derive the step responses of RL and RC circuits. Compare their performances. **(16)**

(OR)

- b) Derive an expression for the current response of RLC series circuit with sinusoidal excitation. Assume that the circuit is working in critical damping condition. **(16)**

15. a) Define power, power factor. Explain the two Wattmeter method of measuring power in 3-phase circuits with neat sketch. **(16)**

(OR)

- b) Derive the current, voltage and power equation for the star connection system and delta connection system. **(16)**
-