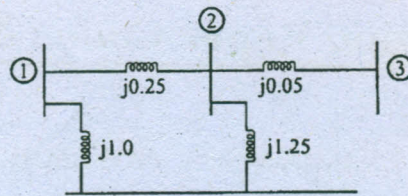


12. (a) (i) Find the bus impedance matrix for the system whose reactance diagram is shown in fig. All the impedances are in p.u. (8)



Reference bus

Fig. 12 (a) (i)


- (ii) Draw the network and find bus admittance matrix. (8)

Bus Code Line Impedance p.u. Line Charging Admittance p.u

1-2	$0.2+j0.8$	$j0.02$
2-3	$0.3+j0.9$	$j0.03$
2-4	$0.25+j 1$	$j0.04$
3-4	$0.2+j0.8$	$j0.02$
1-3	$0.1 +j0.4$	$j0.01$

Or

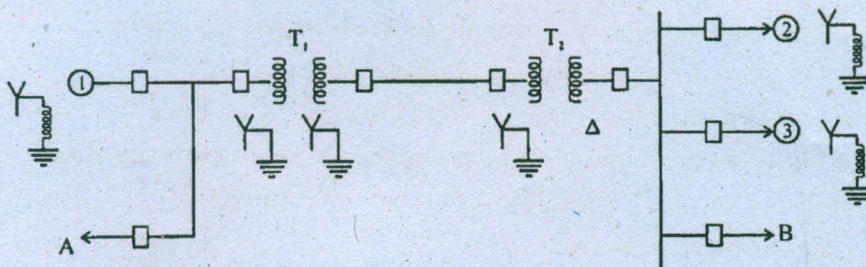- (b) Obtain the p.u. impedance diagram of the power system shown below: (16)



Generator No.1: 30 MVA, 10.5 kV, $X'' = 1.6$ Ohm

Generator No.2: 15 MVA, 6.6 kV, $X'' = 1.2$ Ohm

Generator No.3: 25 MVA, 6.6 kV, $X'' = 0.56$ Ohm

Transformer T1 (3phase) : 15 MVA, 33/11 kV, $X = 15.2$ Ohm per phase on HT side

Transformer T2 (3phase) : 15 MVA, 33/6.8 kV, $X = 16$ Ohm per phase on HT side

Transmission line: 20.5 Ohm/phase

Load A : 15 MW, 11 kV, 0.9 p.f. lagging


Load B : 40 MW, 6.6 kV, 0.85 p.f lagging

13. (a) Derive load flow algorithm using Gauss - Seidel method with flow chart and discuss the advantages of the method. (16)

Or

- (b) Derive load flow algorithm using Newton-Raphson method with flow chart and state the importance of the method. (16)

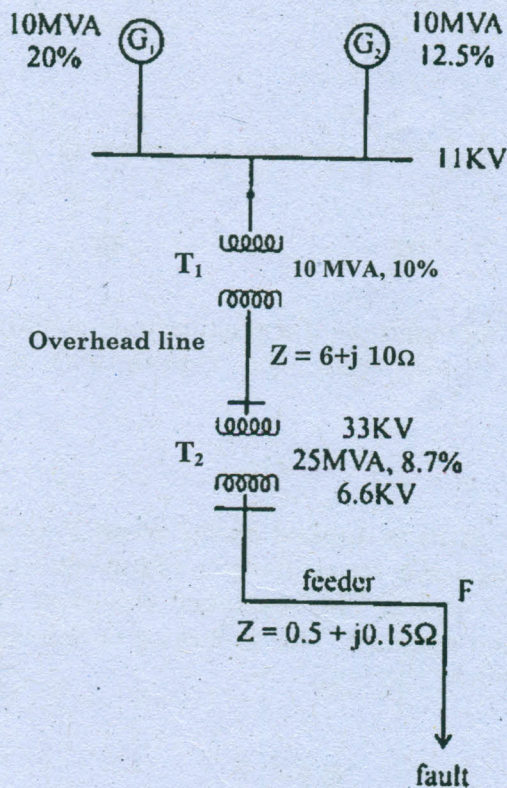
14. (a) (i) For the radial network shown below a three phase fault occurs at point F. Determine the fault current and the line voltage at 11 kV bus under fault conditions. (8)



- (ii) Obtain the symmetrical components of a set of unbalanced currents $I_a = 1.6 \angle 25^\circ$, $I_b = 1.0 \angle 180^\circ$, $I_c = 0.9 \angle 132^\circ$. (8)

Or

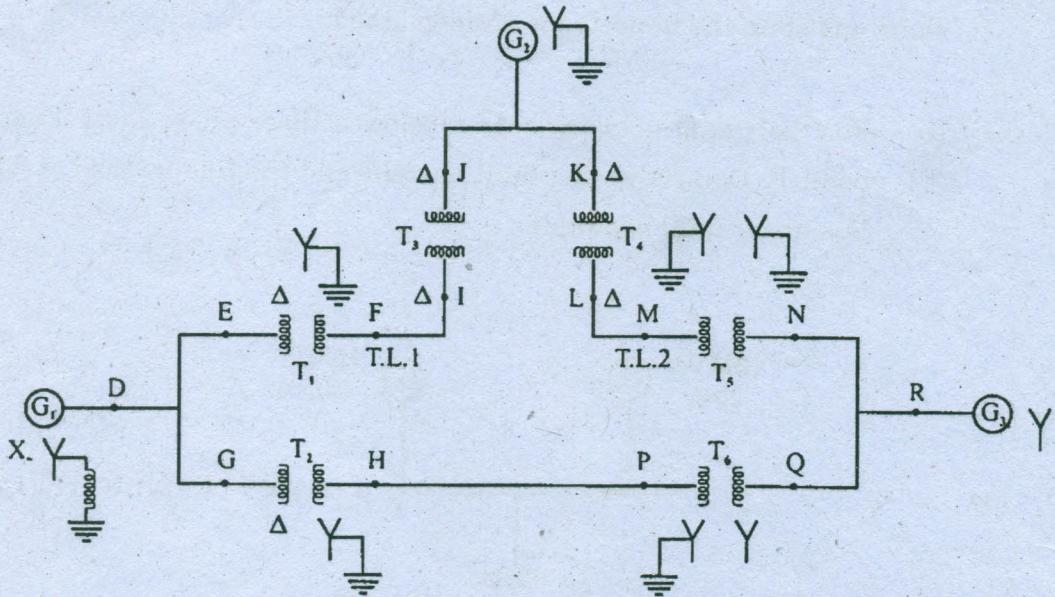- (b) (i) Derive the expression for fault current in double line to ground fault on unloaded generator. Draw an equivalent network showing the inter connection of networks. (10)
- (ii) Draw the zero sequence diagram from the system whose one - line diagram is shown below. (6)



15. (a) Derive the swing equation of a synchronous machine swinging against an infinite bus. Clearly state the assumptions in deducing the swing equation. (16)

Or

- (b) A three phase fault is applied at the point P as shown in Fig. Find the critical clearing angle for clearing the fault with simultaneous opening of the breakers 1 and 2. The reactance values of various components are indicated in the diagram. The generator is delivering 1 p.u power at the instant preceding the fault. (16)

