



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : X10379

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY 2021

Sixth Semester

Electrical and Electronics Engineering

EE8004 – MODERN POWER CONVERTERS

(Regulations 2017)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What is the main advantage of resistance emulation technique ?
2. What are the advantages of DCM ?
3. Define displacement factor.
4. What are the effects of saturation of supply transformer ?
5. List the advantages of MLIs over conventional VSIs.
6. Redundant switching states.
7. Define inter-harmonics.
8. What is scalar modulation ?
9. Define EMI.
10. Differentiate ZVT from ZCT.



11. a) i) Detail the SMPS circuits with and without isolation using suitable example. (6)
- ii) Design a Buck-Boost converter circuit having parameters, input voltage = 24V, $D = 0.4$, load resistance = 5 ohm, $L = 20\text{mH}$, $C = 80\text{mF}$. Determine the output voltage, average inductor current, Maximum and minimum value of inductor current, Maximum and minimum value of inductor current and the output voltage ripple. Assume a switching frequency of 100 kHz. (7)
- (OR)
- b) i) The forward converter has the following parameters : (9)
- $V_d = 48\text{V}$, $R_L = 10\Omega$, output inductor = 0.5mH, $C = 100\mu\text{F}$, $t_s = 35\text{kHz}$, $N_1/N_3 = 1.5$, $N_1/N_2 = 1$, $D = 0.4$, $L_m = 5\text{mH}$.
- A) Determine the output voltage, maximum and minimum currents in the inductor and peak to peak output voltage ripple.
- B) Determine the peak current in the transformer primary winding.
- ii) Discuss the closed loop performance of the SMPS circuits. (4)
12. a) Explain how the efficiency of AC/DC converters can be improved through Synchronous Rectification. (13)
- (OR)
- b) i) Compare the performance of AC/DC converters with and without isolation. (6)
- ii) Discuss how a boost converter can be used for PFC in ac-dc converters. (7)
13. a) i) Explain with the help of the mode diagrams, the working of flying capacitor MLI. (8)
- ii) Discuss the principle of multicarrier PWM methods suitable for MLI. (5)
- (OR)
- b) i) Enumerate the working principle of cascaded H-Bridge multilevel inverter with the help of suitable diagrams. (9)
- ii) Compare all three basic MLI topologies. (4)
14. a) i) Discuss the operation and control of the matrix converter. (8)
- ii) Provide the performance comparison of matrix converter with DC link converters. (5)
- (OR)
- b) i) Enumerate how the SVM can be used to control matrix converter. (8)
- ii) Explain how the matrix converter can be operated as AC-DC converter. (5)



15. a) i) Explain the operation of zero current switching Quasi-resonant boost converter with neat circuit and waveforms. **(8)**
ii) Draw and explain a typical resonant converter based SMPS. **(5)**

(OR)

- b) i) Explain the operation of class E Resonant inverter. **(7)**
ii) The Zero Current Resonant Converter (ZCS) delivers a maximum power $P_L = 400\text{mW}$ at $V_o = 4\text{V}$. The supply voltage $V_s = 15\text{V}$, the maximum operating frequency is $f_{\text{max}} = 50\text{ kHz}$. Determine the values of L and C. Assume that the intervals t_1 and t_3 are very small and $x = 1.5$. **(6)**

PART – C

(1×15=15 Marks)

16. a) i) Develop a SVPWM scheme for a NPC inverter and include the state vector diagram in the discussion. **(10)**
ii) Consider a buck converter with a dc voltage source of 80V and a load resistance equal to 18Ω . It is required that this converter deliver at least 100W to the load. Assume the switching frequency is 150kHz. Determine (a) the inductor critical value, L_{crit} , (b) the voltage gain for $L = 0.1 L_{\text{crit}}$ and $10L_{\text{crit}}$, (c) DI for $L = 0.1 L_{\text{crit}}$, and the maximum inductor current at $t = DT$. **(5)**

(OR)

- b) i) Explain the Venturini method applicable to matrix converter. **(10)**
ii) With the help of switching loci explain zero voltage and zero current switching. **(5)**
-