

30/11 FN
Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 66271

M.E. DEGREE EXAMINATION, DECEMBER 2015/JANUARY 2016

First Semester

Power Electronics and Drives

PX7102 : ANALYSIS OF POWER CONVERTERS

(Common to M.E. Control and Instrumentation Engineering)

(Regulations – 2013)

Time : Three Hours

Maximum : 100 Marks

Answer ALL Questions.

PART – A (10 × 2 = 20 Marks)

1. Write short note on blocking condition of a diode.
2. How are gate turn of thyristors turned on and off ?
3. Define Modulation Index.
4. Does the commutation angle depend on the delay angle of converters ?
5. Write the principle of operation of step down chopper.
6. What are the effects of chopping frequency on filter sizes ?
7. Write short note on tie control arrangement.
8. Mention the advantages of delta connected controllers.
9. Write the principle of operation of cycloconverters.
10. What is meant by matrix converters ?

PART – B (5 × 13 = 65 Marks)

11. (a) Explain the concept of extinction angle control of commutation technique of converters.

OR

- (b) Demonstrate the operation of single phase fully controlled converters during RLE loads with its characteristics.

12. (a) With a neat sketch, explain the operation and characteristics of three phase dual converter.

OR

- (b) Illustrate the operation of three phase half controlled converter with free wheeling diodes.

13. (a) Demonstrate the operation and characteristics of step up DC chopper with RL load.

OR

- (b) Derive necessary equations and explain the operation of buck boost converters with its advantages.

14. (a) Explain the operation of phase control technique with neat sketch.

OR

- (b) Demonstrate the operation of single phase bidirectional controller with RL loads.

15. (a) With neat sketch, illustrate the operation of three phase dual converters.

OR

- (b) Explain the operation and characteristics of single phase cycloconverter with neat sketch.

PART – C (1 × 15 = 15 Marks)

16. (a) A three phase full converter is supplied from a three phase 230 V, 60 Hz supply. The load current is continuous and has negligible ripple. If the average load current $I_{dc} = 125$ A and the commutating inductance $L_c = 0.1$ mH, determine the overlap angle when (a) $\alpha = 15^\circ$, (b) $\alpha = 30^\circ$ and (c) $\alpha = 65^\circ$.

OR

- (b) A highly inductive load is controlled by a chopper. The average load current $i_a = 100$ A and the load ripple current can be considered negligible ($\Delta I = 0$). A simple LC input filter with $L_e = 0.3$ mH and $C_e = 4500$ μ F is used. If the chopper is operated at a frequency of 350 Hz and a duty cycle of 0.5, determine the maximum RMS value of the fundamental component of chopper-generated harmonic current.